

Department of Electrical and Electrical Engineering, SEET, FUTA.

Course code/Title: EEE 305/307/351 – Electrical Machines 1 Session: 2023/2024 Date: 3 May, 2024

Instruction: Answer all questions

1. With the aid of good diagrams and two examples explain what you understand by singly and multiply excited systems (6mks)
2. A 200 kVA rated transformer has a full-load copper loss of 2 kW and iron loss of 1.5 kW. Determine the transformer efficiency at (a) full load (b) half full load 0.85 P.f
3. An 8-pole d. c. generator has a lap-wound armature with 1200 conductors. The useful flux per pole is 20 mWb. Find the torque exerted when a current of 20 A flows in each conductor.



THE FEDERAL UNIVERSITY OF TECHNOLOGY, AKURE
School of Engineering and Engineering Technology

Department of Electrical and Electronics Engineering
B. Eng. 1st Semester 2023/2024 Examination

EEE305/307*/351* – Electrical Machines I

Date: 18/05/2024

Instruction: Answer number 1 and any other three questions

Time: 2 $\frac{1}{4}$ Hrs

Question 1 ✓

- (a) With the aid of good diagrams and two examples explain what you understand by singly and multiply excited systems (6mks)
- (b) A 500 kVA rated transformer has a full-load copper loss of 3 kW and iron loss of 2 kW. Determine the transformer efficiency at (a) full load and 0.8 (b) half full load and 0.8 (7 mks)
- (c) An 8-pole d. c. generator has a wave-wound armature with 1500 conductors. The useful flux per pole is 20 mWb. Determine (a) the e. m. f. generated when running at 500 rpm, and (b) torque exerted when a current of 20 A flows in each conductor (7 mks)

$$T = \frac{P_{\phi Z}}{\omega_c} =$$

Question 2

- (a) How can the effect of poor commutation in dc machines be improved? (3 mks)
- (b) A 4 kVA 400/200 V, 50 Hz single phase transformer has the following test data:
 - O. C. test; 200 V, 1 A, 64 W
 - S. C. test; 15 V, 10 A, 80 W. Determine:
- (i) equivalent circuit parameters referred to the L. V. side; and
- (ii) secondary load voltage on full load at 0.8 p. f. lagging (12 mks)

Question 3 ✓

- (a) Explain with appropriate diagrams the two types of transformer construction (5 mks)
- (b) A transformer has 600 primary turns and 200 secondary turns. The primary and secondary resistances are 0.25Ω and 0.010Ω respectively and corresponding leakage reactances are 2Ω and 0.08Ω respectively. Determine:
 - (i) the equivalent resistance referred to the primary winding;
 - (ii) the equivalent reactance referred to the primary winding;
 - (iii) the equivalent impedance referred to the primary winding;
 - (iv) the phase angle of the impedance

(10 mks)

$$\frac{200 \times 2}{c} = \frac{P_{\phi Z}}{\omega_c}$$

Question 4 ✓

- (a) A three-phase transformer has 600 primary turns and 50 secondary turns. If the supply voltage is 5 kV. Find the secondary line voltage on no-load when the windings are connected (a) star-delta, (b) delta-star. (7 mks)
- (b) A shunt dc generator supplies a 24 kW load at 200 V through cables of resistance,

$$\begin{array}{l} P.D.a \\ S.T. \\ 600 \\ V = 5KV \end{array} \quad \begin{array}{l} S.C. \\ Delta \\ 50 \\ V_2? \end{array}$$

Question 5

- ### Question 6

- 290kV.
-
- The diagram shows a parallel plate capacitor. The top plate is connected to a terminal labeled '1' and the bottom plate to a terminal labeled '2'. A dielectric slab, represented by a rectangle with diagonal lines, is partially inserted between the plates. To the left of the capacitor, there is a label 'g' and two horizontal lines with arrows pointing towards each other, indicating the gap or distance between the plates.

Fig Q₆